

AC Circuits


Dr. Nahla Zakzouk

The response of the basic elements R,L, and C to a sinusoidal voltage or current


I. Resistor

The resistive impedance Z_R is given by;

$$\therefore Z_R = R \quad (\Omega)$$

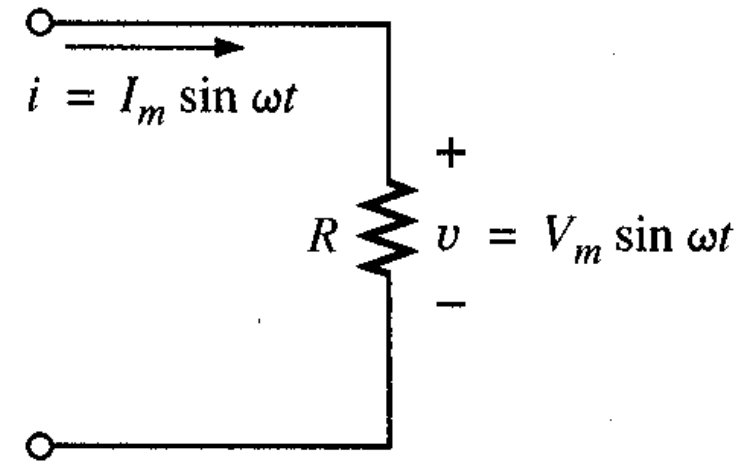

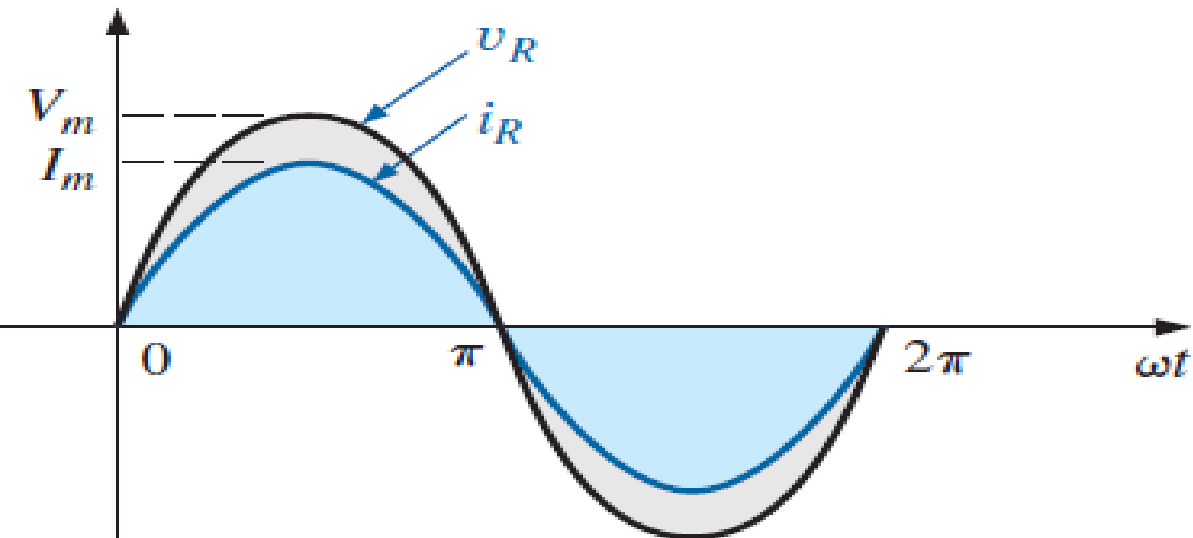The voltage and current of a pure resistive element are in phase.



II. Inductor



The quantity ωL , is called the inductive reactance, X_L

$$X_L = \omega L = 2\pi f L \quad (\Omega)$$

The inductive impedance Z_L is given as:

$$Z_L = jX_L = j\omega L = \omega L \angle 90^\circ (\Omega)$$

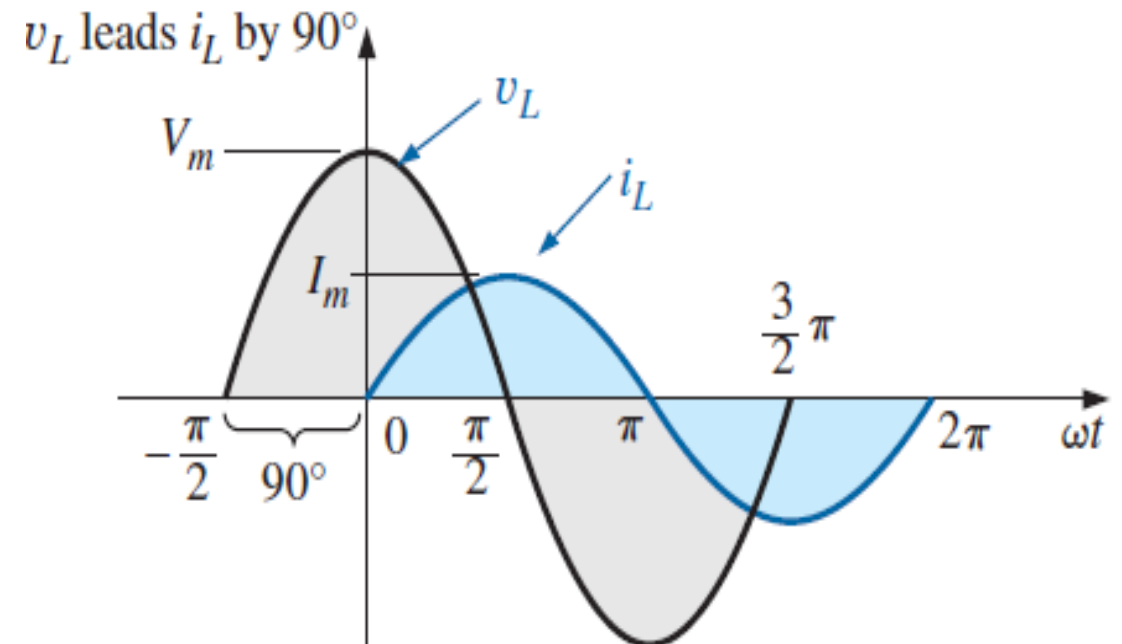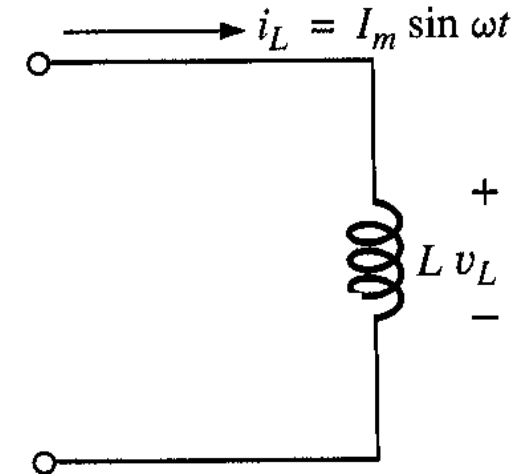For a pure inductor, the current through the coil lags the voltage across the coil by 90°





III. Capacitor

The quantity $1/\omega C$, called the **capacitive reactance**, $\underline{X_C}$

$$\underline{X_C} = \frac{1}{\omega C} = \frac{1}{2\pi f C} \quad (\Omega)$$

The **capacitive impedance** $\underline{Z_C}$ is given as:

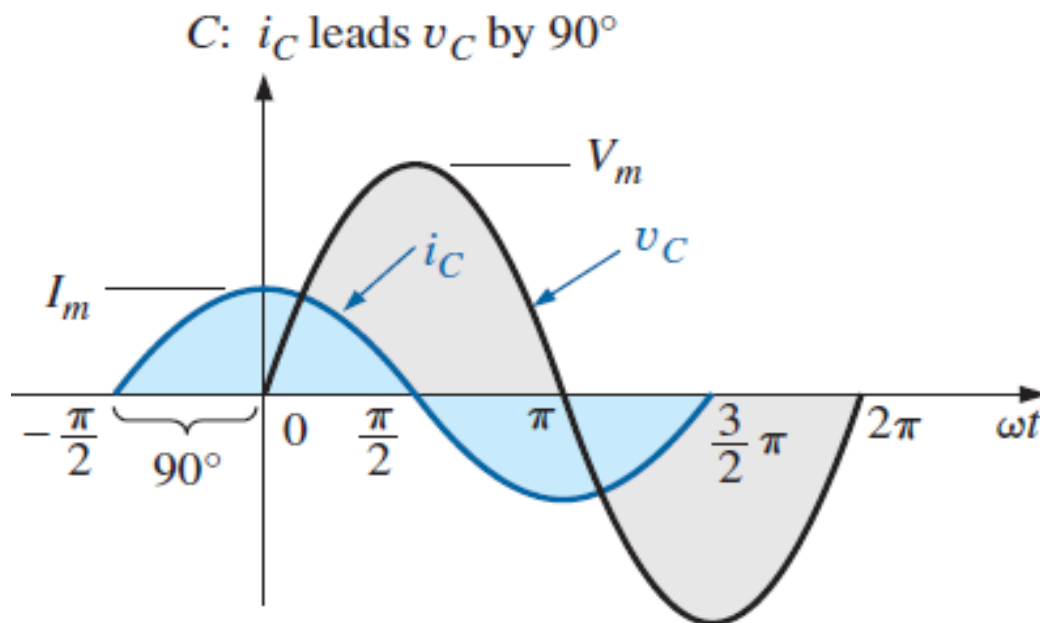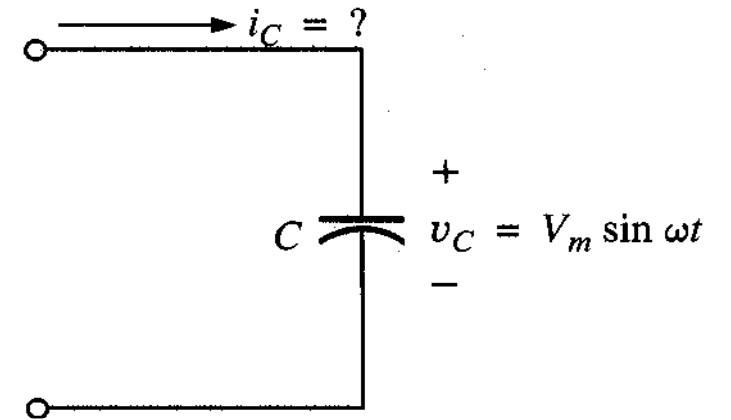
$$\therefore \underline{Z_C} = -jX_C = -j\frac{1}{\omega C} = \frac{1}{\omega C} \angle -90^\circ \quad (\Omega)$$





For a pure capacitor, the current through the capacitor leads the voltage across it by 90° .

RLC Circuits


If $v = V_m \sin(\omega t + \varphi) \rightarrow \rightarrow \rightarrow \therefore V = V_{rms} \angle \varphi \rightarrow \rightarrow \rightarrow I = \frac{V}{Z_T} = \frac{V_{rms} \angle \varphi}{|Z_T| \angle \theta} = |I| \angle (\varphi - \theta)$

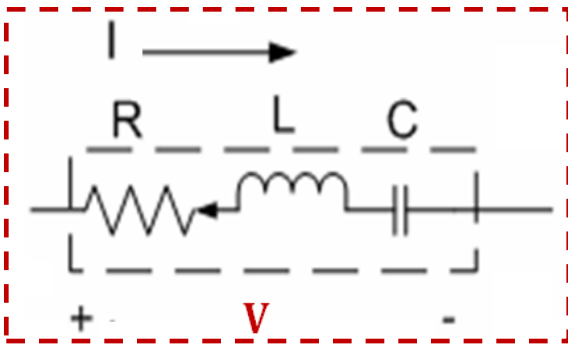

Total impedance, $Z_T = R + jX_L - jX_C = R + j(X_L - X_C)$
 $Z_T = R + j\left(\omega L - \frac{1}{\omega C}\right) = |Z_T| \angle \theta$

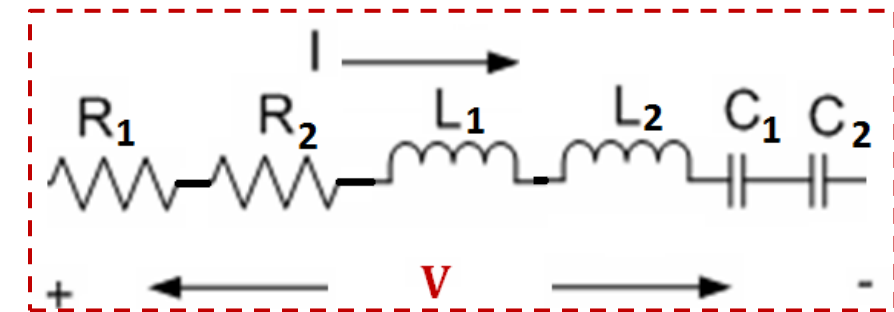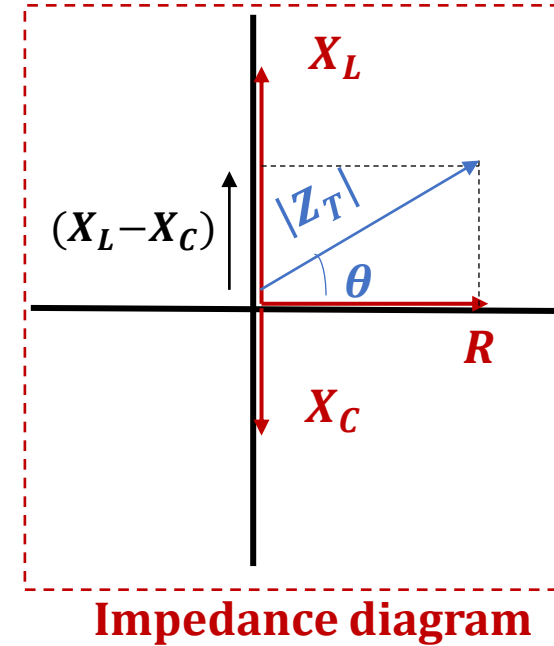

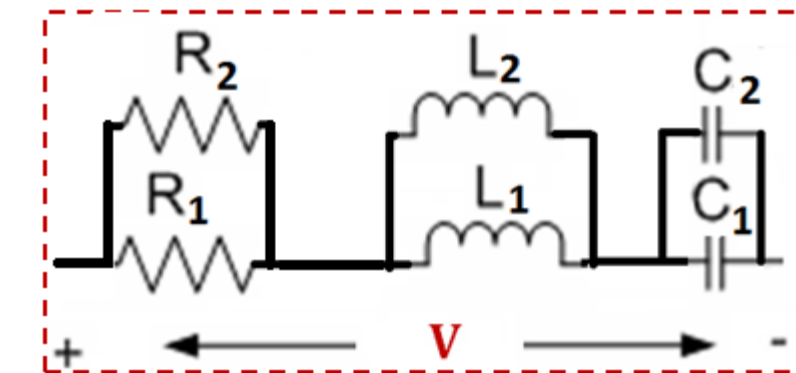
$R_T = R_1 + R_2$
 $L_T = L_1 + L_2 \rightarrow \rightarrow X_{L_T} = \omega L_T$
 $C_T = \frac{C_1 \times C_2}{C_1 + C_2} \rightarrow \rightarrow X_{C_T} = \frac{1}{\omega C_T}$
 Total impedance, $Z_T = R_T + jX_{L_T} - jX_{C_T}$



$R_T = \frac{R_1 \times R_2}{R_1 + R_2}$
 $L_T = \frac{L_1 \times L_2}{L_1 + L_2} \rightarrow \rightarrow X_{L_T} = \omega L_T$
 $C_T = C_1 + C_2 \rightarrow \rightarrow X_{C_T} = \frac{1}{\omega C_T}$
 Total impedance, $Z_T = R_T + jX_{L_T} - jX_{C_T}$

Impedances connections

I. Series connection

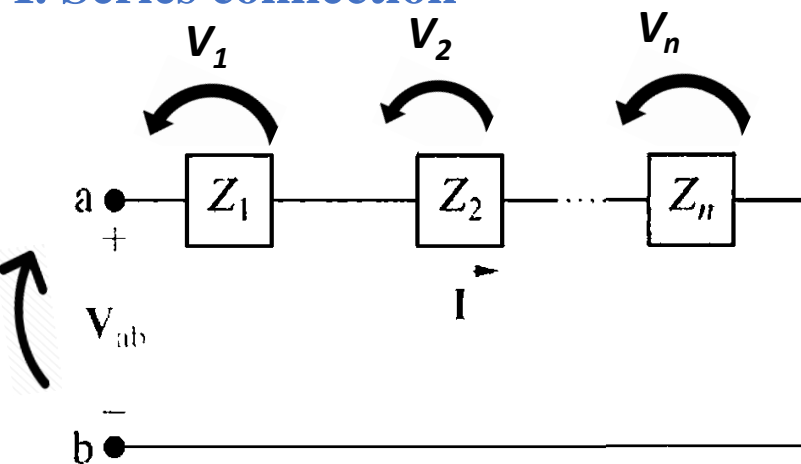

Applying K.V.L.

$$V_{ab} = V_1 + V_2 + \dots + V_n$$

$$\begin{aligned} V_{ab} &= Z_1 I + Z_2 I + \dots + Z_n I \\ &= (Z_1 + Z_2 + \dots + Z_n) I. \end{aligned}$$


The equivalent impedance between terminals a, b is

$$Z_{ab} = \frac{V_{ab}}{I} = Z_1 + Z_2 + \dots + Z_n$$

Applying voltage divider

$$V_1 = V_{ab} \frac{Z_1}{Z_{ab}}, V_2 = V_{ab} \frac{Z_2}{Z_{ab}} \dots \dots \dots, V_n = V_{ab} \frac{Z_n}{Z_{ab}}$$

II. Parallel connection

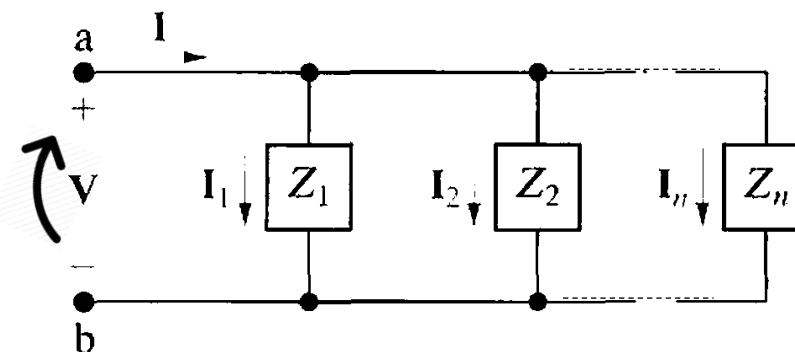

Applying K.C.L.

$$I = I_1 + I_2 + \dots + I_n,$$

$$\frac{V}{Z_{ab}} = \frac{V}{Z_1} + \frac{V}{Z_2} + \dots + \frac{V}{Z_n}.$$

The equivalent impedance between terminals a, b is

$$\frac{1}{Z_{ab}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n} \quad \begin{array}{l} \text{For only 2} \\ \text{impedances in parallel} \end{array} \quad \Rightarrow \quad Z_{ab} = \frac{Z_1 Z_2}{Z_1 + Z_2},$$


Applying current divider

$$I_1 = I \frac{Z_{ab}}{Z_1}, I_2 = I \frac{Z_{ab}}{Z_2} \dots \dots \dots I_n = I \frac{Z_{ab}}{Z_n}$$

$$\begin{array}{l} \text{For only 2} \\ \text{impedances in parallel} \end{array} \quad \Rightarrow \quad \begin{aligned} I_1 &= I \frac{Z_2}{Z_1 + Z_2} \\ I_2 &= I \frac{Z_1}{Z_1 + Z_2} \end{aligned}$$

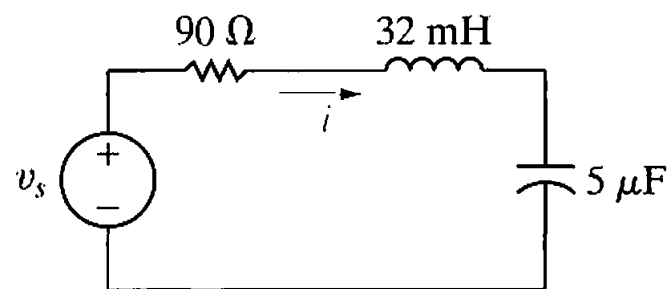Problem 1

The steady-state expression for the source voltage v_s is $750 \cos(5000t + 30^\circ)$, get i



Solution

From the expression for v_s , $\omega = 5000\text{ rad/s}$

$$Z_L = j\omega L = j(5000)(32 \times 10^{-3}) = j160\ \Omega$$

$$Z_C = j \frac{-1}{\omega C} = -j \frac{10^6}{(5000)(5)} = -j40\ \Omega$$

$$\begin{aligned} Z_T &= 90 + j160 - j40 \\ &= 90 + j120 = 150 \angle 53.13^\circ\ \Omega \end{aligned}$$

The phasor transform of v_s is


$$\mathbf{V}_s = 750 \angle 30^\circ\text{ V}$$

$$\mathbf{I} = \frac{750 \angle 30^\circ}{150 \angle 53.13^\circ} = 5 \angle -23.13^\circ\text{ A}$$

$$i = 5 \cos(5000t - 23.13^\circ)\text{ A}$$

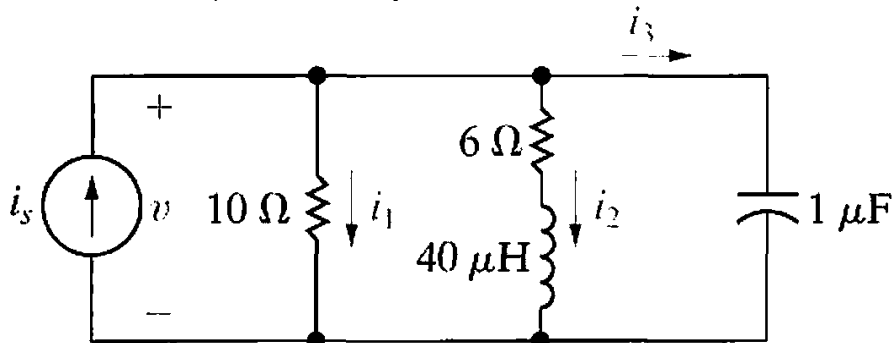Problem 2

The steady-state expression for the source current, i_s is $8 \cos(200,000 t)$ A get v , i_1 , i_2 , and i_3



Solution

$$\omega = 200,000\ \text{rad/s}$$

$$Z_L = j\omega L = j8\ \Omega$$

$$Z_C = j\frac{-1}{\omega C} = -j5\ \Omega$$

$$\begin{aligned}\frac{1}{Z} &= \frac{1}{10} + \frac{1}{6 + j8} + \frac{1}{-j5} \\ &= 0.2 \angle 36.87^\circ\ \text{S}\end{aligned}$$

$$Z = 5 \angle -36.87^\circ\ \Omega.$$

The phasor transform of i_s is

$$\mathbf{I} = 8 \angle 0^\circ$$

The Voltage \mathbf{V} is

$$\mathbf{V} = Z\mathbf{I} = 40 \angle -36.87^\circ\ \text{V}.$$

Hence

$$\mathbf{I}_1 = \frac{40 \angle -36.87^\circ}{10} = 4 \angle -36.87^\circ = 3.2 - j2.4\ \text{A}$$

$$\mathbf{I}_2 = \frac{40 \angle -36.87^\circ}{6 + j8} = 4 \angle -90^\circ = -j4\ \text{A},$$

and

$$\mathbf{I}_3 = \frac{40 \angle -36.87^\circ}{5 \angle -90^\circ} = 8 \angle 53.13^\circ = 4.8 + j6.4\ \text{A}$$

The corresponding steady-state time expressions are

$$v = 40 \cos(200,000t - 36.87^\circ)\ \text{V},$$

$$i_1 = 4 \cos(200,000t - 36.87^\circ)\ \text{A},$$


$$i_2 = 4 \cos(200,000t - 90^\circ)\ \text{A},$$

$$i_3 = 8 \cos(200,000t + 53.13^\circ)\ \text{A}.$$

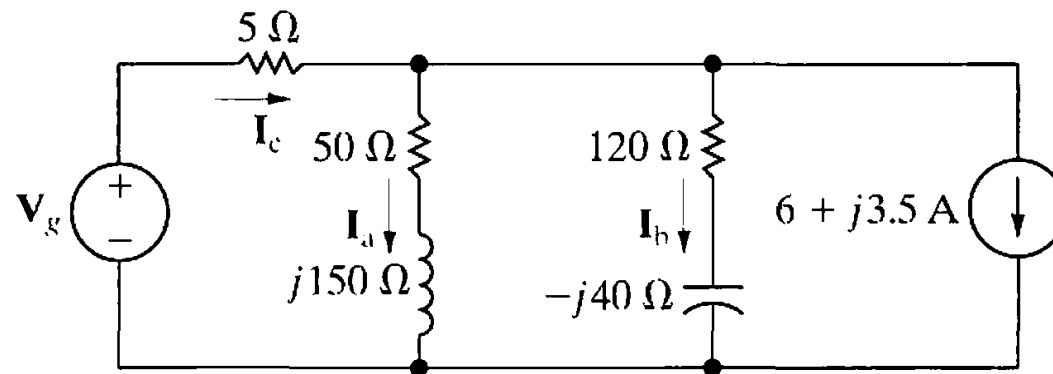Problem 3

The phasor current \mathbf{I}_a in the circuit shown in Fig. P9.33 is $2\angle 0^\circ$ A.

- Find \mathbf{I}_b , \mathbf{I}_c , and \mathbf{V}_g .
- If $\omega = 800$ rad/s, write the expressions for $i_b(t)$, $i_c(t)$, and $v_g(t)$.



Solution

[a] $\mathbf{V}_a = (50 + j150)(2\angle 0^\circ) = 100 + j300$ V


$$\mathbf{I}_b = \frac{100 + j300}{120 - j40} = j2.5$$
 A

K.C.L.

$\mathbf{I}_c = 2\angle 0^\circ + j2.5 + 6 + j3.5 = 8 + j6$ A

K.V.L.

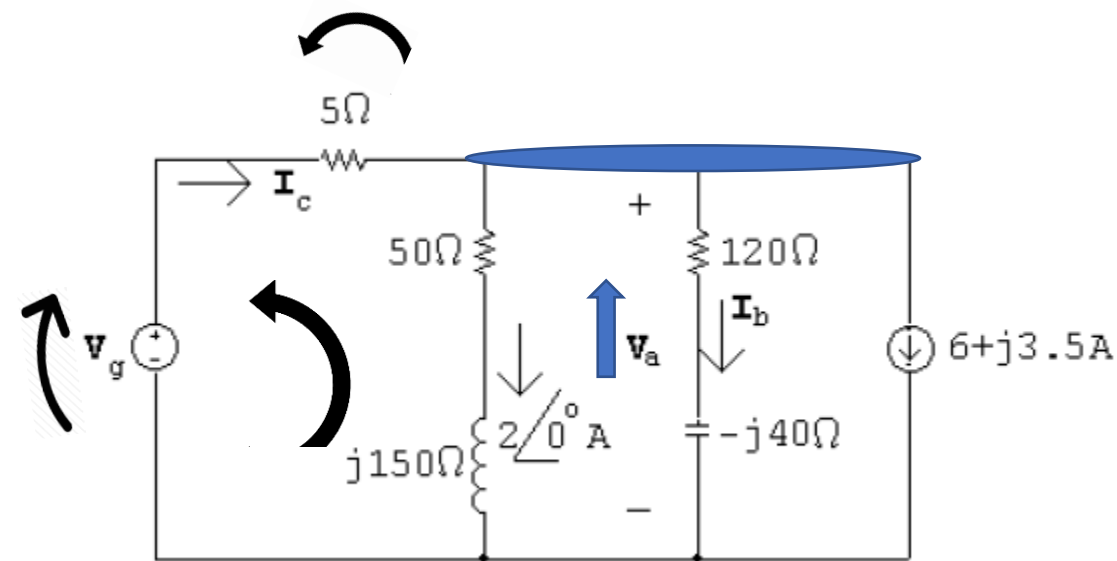$\mathbf{V}_g = 5\mathbf{I}_c + \mathbf{V}_a = 5(8 + j6) + 100 + j300 = 140 + j330$ V



[b] $i_b = 2.5 \cos(800t + 90^\circ)$ A

$$i_c = 10 \cos(800t + 36.87^\circ)$$
 A

$$v_g = 358.47 \cos(800t + 67.01^\circ)$$
 V

Report

Find \mathbf{I}_b and \mathbf{Z} in the circuit shown in Fig. P9.32 if $\mathbf{V}_g = 25 \angle 0^\circ \text{ V}$ and $\mathbf{I}_a = 5 \angle 90^\circ \text{ A}$.

